

## **UNIT 1 2 MARKS QUESTIONS**

Q 1 Explain MESH and LOOP .

Q 2 Explain NODE and JUNCTION.

Q 3 Explain active and passive element.

Q 4 Explain unilateral and bilateral element.

Q 5 Explain ideal and practical, current source and voltage source.

Q 6 What are the basic elements of an electrical network?

Q 7 State KVL and KCL .

Q 8 Differentiate between EMF and potential difference.

Q 9 Why linearity is important.

Q 10 Explain linear and non linear element.

Q 11 Explain lumped and distributive network.

## Unit 2 , 2 MARKS QUESTION

Q 1 What are the value of power factor for

i) pure resististive circuit

ii) pure inductive circuit

iii) pure capacitive circuit

define it.

Q 2 what is the average power of pure Inductive and pure capacity circuit.

Q 3 Define the term "Dynamic Impedance" in AC circuit.

Q 4 Define power factor and quality factor

Q 5 Why series resonance circuit is known as acceptor circuit and parallel resonant circuit is known as rejector circuit.

Q 6 What is the relationship between line and phase, voltage and current for a e phase star and delta connection balance system.

Q 7 What do you mean by active power, reactive power and Apparent power.

Q 8 What do you mean by form factor and peak factor.

Q 9 What do you mean by average and RMS value.

Q 10 What are the causes of low power factor and how can we improve it.

UNIT-3 - 2-Marks Questions

- Q-1 Explain (i) Reluctance (ii) Permeability (iii) Magnetic field Density (iv) Magnetic field Strength.
- Q-2 What happens if D.C supply is given to the Transformer.
- Q-3 What do you mean by Voltage Regulation of Transformer.
- Q-4 Why Transformer are rated in KVA not in KW?
- A-4 Iron loss depends on voltage & Copper loss depends on current of a transformer, Hence, total transformer heat loss depends on Volt-Ampere (VA) & independent of phase angle among voltage & current.
- Q-5 State different losses in Transformer.
- Q-6 Give the expression for the load current, when the transformer operates at its maximum efficiency.
- Q-7 Compare Core type & Shell Type Transformer.
- Q-8 Explain Magnetic Leakage & Fringing.
- Q-9 Compare Electric & Magnetic Circuits.
- Q-10 Write different types of Magnetic Material.



## UNIT-4 , 2-Mark Questions

Q-1 Give classification of D.C. Machines.

Q-2 What do you mean by Back EMF.

Q-3 What is generated EMF in D.C. Generator.

Q-4 What will happen, if the field winding of a running D.C. shunt motor suddenly opens/short?

A-4

$$T \propto \phi I_a$$

$$T \propto \frac{1}{N}$$

① If motor is short circuited.  
then,  $I_a = 0$ ,  $T = 0$ .  
Motor will stop rotating.

② If motor is at open  
 $\phi$  will decrease,  $\therefore N$  increases to maintain constant  $E_b$ .  
 $\therefore E_b \propto N \phi \downarrow$   
 $\therefore$  Speed will dangerously increase.

Q-5 What is the function of Brushes in D.C. Machine?

Q-6 How can we change the direction of rotation of D.C. Motor?

Q-7 What is the role of commutator in D.C. Machine?

Q-8 Why D.C. series motor is never started on No-Load.

Q-9 Write applications of synchronous motor.

Q-10 Can Induction Motor run at synchronous speed? Justify your answer.

Q-11 Why condenser is used in a single-phase Induction Motor?

Q-12 Enlist the various methods of starting of a 1- $\phi$  Induction Motor?

Q-13 Write applications of single-phase induction motor.

Q-14 Give the expression of speed in terms of poles & freq. of supply

Q-15 What is the function of slip rings in a 3- $\phi$  Induction Motor.

Q-16 What is called synchronous speed in AC Machines.



UNIT-5 . 2 Marks Questions

- Q-1 Write full forms of (i) SFU, (ii) MCB, (iii) MCCB, (iv) AEB  
(v) ELCB.
- Q-2 What is the difference between Primary & Secondary Batteries?
- Q-3 What is the necessity of Earthing?
- Q-4 Why Earth pin is made thicker and bigger than Line & neutral?
- Q-5 What are the factors that affect the battery capacity?
- Q-6 What do you mean by Burbar?