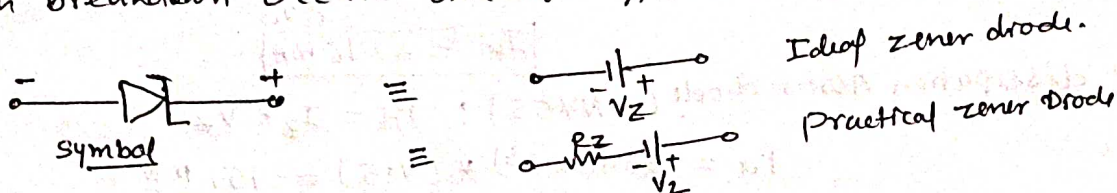



## Zener Diode :

- (\*) A device which work in Reverse biased region as a constant voltage source.
- (\*) The Zener diode having low breakdown voltage because of it is heavily doped diode. Breakdown in which breakdown occurs due to Zener process.
- (\*) Zener diode having high breakdown voltage, lightly doped diodes in which breakdown occurs due to Avalanche process.


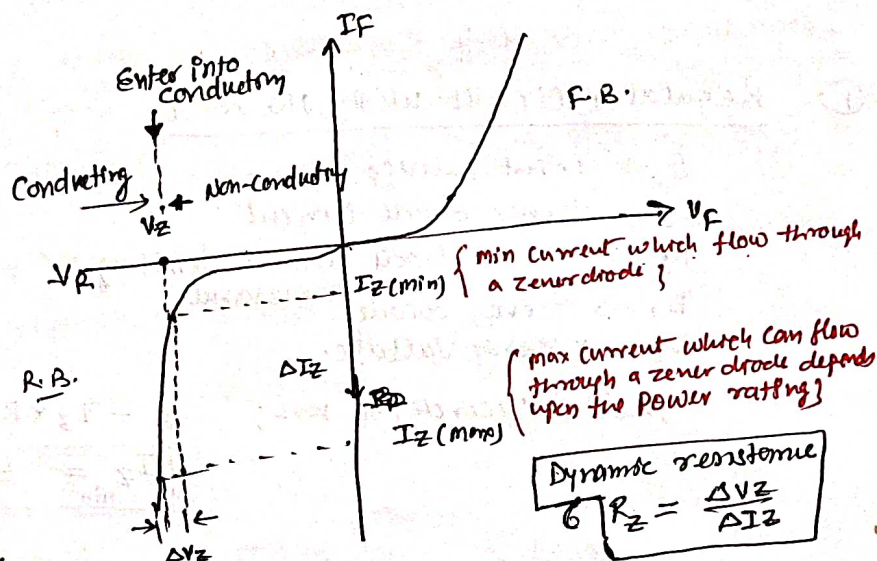
## Characteristics

- (\*) Zener diode is same as normal diode in forward bias.
- (\*) The region of characteristics in R.B. where Zener current can increase or decrease but voltage remains constant at  $V_Z$  is known as breakdown region.



- (\*) When Zener diode is reverse biased below the breakdown voltage, current is practically zero & Zener diode is non-conducting & is working as a normal diode.

- (\*) When reverse voltage equals to breakdown voltage, the current through the Zener diode suddenly increases to  $I_Z^+$  this is due to the breakdown phenomena & Zener diode enter into conduction.

- (\*) When reverse voltage <sup>are</sup> greater than breakdown voltage then more & more current will be passing into the Zener diode but the voltage drop across the Zener diode will be maintaining constant.

- (\*) To control the reverse current in Zener diode, ~~resistor~~ in reverse biased a series resistance is connected with Zener, is known as current limiting resistor.

- (\*) The Zener diode may be operated at any (Reverse) current level between  $I_{Z(min)}$  or  $I_{ZK}$  to  $I_{Z(max)}$  or  $I_{ZM}$ . When the max current rating is not given then calculated by -

$$P_d = V_Z I_{ZM}$$

$$\text{or } I_{ZM} = \frac{P_d}{V_Z}$$


where  $P_Z \rightarrow$  power rating of Zener diode

$V_Z \rightarrow$  voltage across Zener diode

$I_{ZM} \rightarrow$  max Zener current.



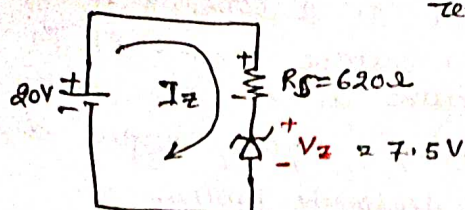Calculate the diode current and power dissipation for given ckt. the Zener Voltage for Zener 1N755 is 7.5V



According to KVL

$$20 - I_Z \times 620 - 7.5 = 0$$

$$I_Z = \frac{20 - 7.5}{620}$$

$$I_Z = 20.16 \text{ mA}$$

Power dissipation across diode (1N755);  $P_d = I_Z \times V_Z$

$$P_d = (20.16 \times 10^{-3}) \times (7.5) = \underline{151 \text{ mW}}$$

### Zener Diode As Voltage Regulator

#### ① Regulator circuit with NO load

$E_S \rightarrow$  Input voltage

$I_Z \rightarrow$  Zener diode current


$R_S \rightarrow$  Zener diode current limiting

$D_1 \rightarrow$  Zener diode



$V_Z \rightarrow$  Zener voltage

Then According to KVL;  $E_S - I_Z \times R_S - V_Z = 0$
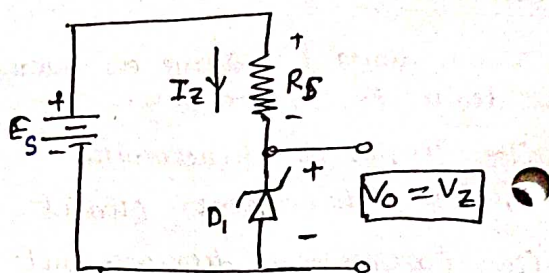
$$I_{Z \text{ min}} = \frac{E_S - V_Z}{R_S}$$



#### ② Loaded Regulator

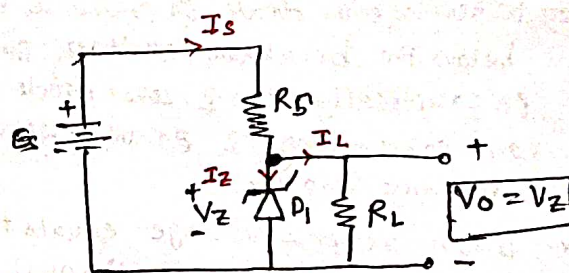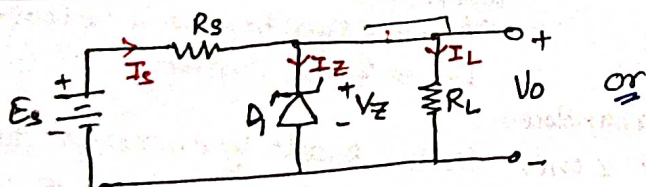

$E_S \rightarrow$  Unregulated supply voltage

$R_S \rightarrow$  Series current limiting resistance

$V_Z \rightarrow$  Zener voltage

$R_L \rightarrow$  Load resistance

$I_Z \rightarrow$  Zener diode current

$I_L \rightarrow$  Load current

$$I_S = I_Z + I_L \quad V_O = V_Z = \left( \frac{R_L}{R_S + R_L} \right) E_S$$

After conducting

$$E_S - I_S R_S - V_Z = 0$$

$$I_S = \frac{E_S - V_Z}{R_S} \quad \text{or} \quad I_Z + I_L = \frac{E_S - V_Z}{R_S}$$

NOTE

For a given  $I_S$ ; if  $I_L \uparrow$  then  $I_Z \downarrow$  i.e.


$$I_S = I_{Z \text{ min}} + I_{L \text{ max}} \\ I_S = I_{Z \text{ max}} + I_{L \text{ min}}$$

If Zener diode is disconnected then  $V_O$ ;

$$E_S - I_S (R_S + R_L) = 0$$

$$\text{or } I_S = \frac{E_S}{R_S + R_L}$$
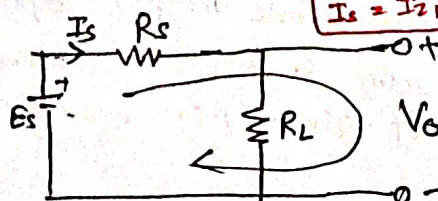
$$\text{and } V_O = I_S \times R_L = \left( \frac{R_L}{R_S + R_L} \right) E_S$$



NOTE:  $V_O$  depends upon the value of  $R_S$ ,  $R_L$  and  $E_S$ . So if these parameters are  $\uparrow$  or  $\downarrow$  then  $V_O$  is also  $\uparrow$  or  $\downarrow$  respectively, i.e.  $V_O$  is unregulated type.



Pr A Circuit will acts as regulator if current through  $R_s$  is atleast  $I_{zmin} + I_L$ .

ie  $I_s \geq I_{zmin} + I_L$

And supply voltage should be sufficient to provide minimum voltage drop across  $R_s$  & voltage  $V_Z$  across the zener diode.

$E_s \geq (I_{zmin} + I_L) R_s + V_Z$

$E_s \geq I_s R_s + V_Z$

### Analysis of zener diode circuit

①  $E_s$  and  $R_L$  both are fixed :

Step-I Determine the state of zener diode by removing the diode from the ckt and calculate the voltage across resulting open circuit.

Step-II Substitute the appropriate equivalent ckt and solve for the desired unknowns.

if  $V > V_Z \rightarrow$  Zener diode (ON)  $\rightarrow$  replace the zener diode by  $V_Z$  voltage source  
if  $V < V_Z \rightarrow$  Zener diode off  $\rightarrow$  replace the zener diode as open circuit.

Step-III When zener diode will be ON, then  $V_L = V_Z$

Step-IV  $I_s = I_Z + I_L$  or  $I_Z = I_s - I_L$


where  $I_s = \frac{E_s - V_L}{R_s}$ ,  $I_L = \frac{V_L}{R_L}$ ,  $R_L(\max) = \frac{V_Z}{I_L(\min)}$

Step-V  $P_Z = V_Z I_Z$

$I_{Zmax} (I_{Zm}) = I_s - I_L(\min)$

$I_L(\min) = I_s - I_{Zm}$


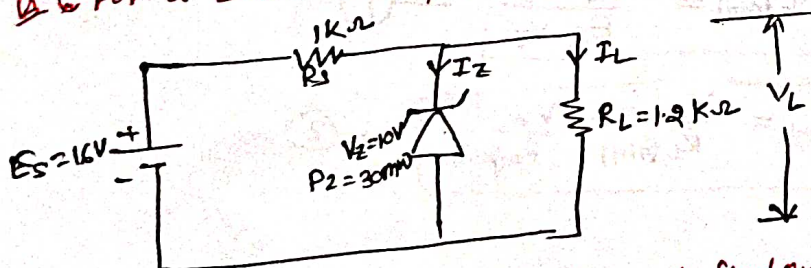
Q For a zener diode, shown below; Find out  $V_L$ ,  $V_R$ ,  $I_Z$ ,  $P_Z$  ② Repeat (1) with  $R_L = 3k\Omega$



Step-I Remove the zener diode and find out voltage

$V = \left( \frac{1.2}{1 + 1.2} \right) * 16 = 8.73V$

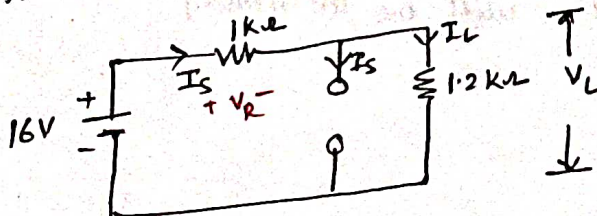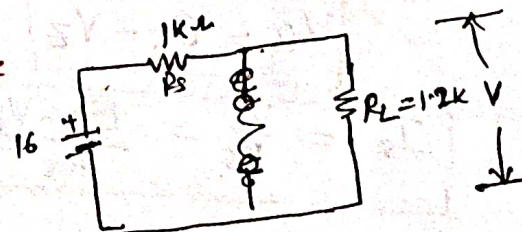Since  $V < V_Z$  ie  $8.73V < 10V \rightarrow$  Zener diode off



Then  $V_L = I_L * 1.2k\Omega = V = 8.73$

But  $V_L = \left( \frac{1.2}{1 + 1.2} \right) * 16 = 8.73$

Then  $I_L = \frac{V_L}{1.2k\Omega} = \frac{8.73}{1.2 * 10^3} = 7.27mA$



But  $E_S - V_R - V_L = 0$

or  $V_R = E_S - V_L = 16 - 8.73 = \underline{7.27V}$

$I_Z = 0A$

$P_Z = V_Z \cdot I_Z = 10 \times 0 = 0 \text{ mW}$

③ If  $R_L = 3k\Omega$

Step-1 Remove zener diode

then  $V = \left( \frac{R_L}{R_S + R_L} \right) \times 16$

$V = \left( \frac{3}{1+3} \right) \times 16 = 12V$

Since  $V > V_Z$  i.e.  $12V > 10V$  then zener diode will be on.

Then  $V_L = V_Z = 10V$


$V_R = E_S - V_L = 16 - 10 = 6V$

$I_L = \frac{V_L}{R_L} = \frac{10}{3} = 3.33 \text{ mA}$

$I_S = \frac{V_R}{R_S} = \frac{6}{1k} = 6 \text{ mA}$

$I_Z = I_S - I_L = 6 \text{ mA} - 3.33 \text{ mA} = 2.67 \text{ mA}$

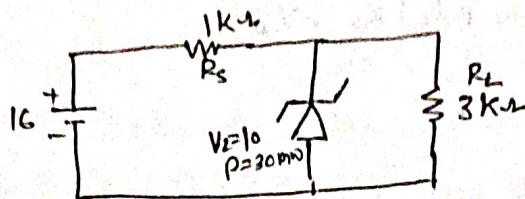$P_Z = V_Z \cdot I_Z = 2.67 \text{ mA} \times 10 = 26.7 \text{ mW}$



## ② Fixed $E_S$ and Variable $R_L$

To find out min load resistance ( $R_L$ ) that will turn on the zener diode i.e.

$V_L = V_Z$

or  $V_L = V_Z = \left( \frac{R_L}{R_S + R_L} \right) \times E_S$  or  $R_S \cdot V_Z + V_Z R_L = R_S E_S$

or  $R_L (E_S - V_Z) = R_S \cdot V_Z$

or  $R_{L(\min)} = \frac{R_S \cdot V_Z}{E_S - V_Z}$  — (1)

$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$  or

$I_{L(\max)} = \frac{V_L}{R_{L(\min)}} = \frac{V_Z}{R_{L(\min)}}$  — (2)

$V_R = E_S - V_Z$

$I_S = \frac{V_R}{R_S} = \frac{E_S - V_Z}{R_S}$  — (3)

$I_Z = I_S - I_L$

If  $I_R$  is fixed then for  $I_{Z(\max)}$ ,  $I_L$  will be minimum

then

$I_{Zm} = I_S - I_{L(\min)}$


$I_{L(\min)} = I_S - I_{Zm}$

$R_{L(\max)} = \frac{V_Z}{I_{L(\min)}}$



Case-II  $E_s \rightarrow \text{Fixed}$ ,  $R_L \rightarrow \text{Variable}$

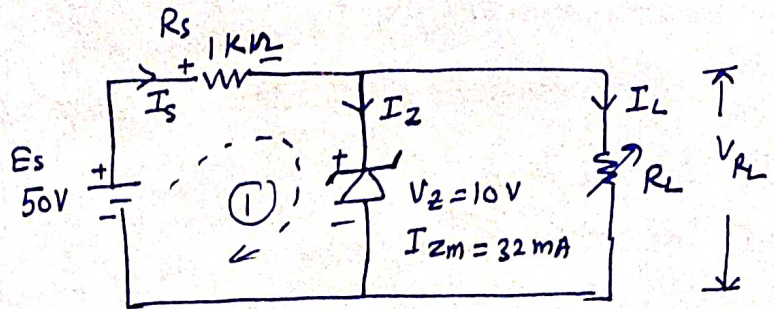- Find out the Range of  $R_L$  &  $I_L$  that will result in  $V_{RL}$  to be maintained at 10 V.
- Determine the max<sup>m</sup> wattage rating of Diode.



Sol<sup>n</sup> Step-I Find out  $R_{L \min}$  that turn on the zener.

When Zener is ON then voltage across load ( $R_L$ ) =  $V_z$

$$V_{RL} = V_z = \left( \frac{R_L}{R_L + R_s} \right) * E_s = \left( \frac{R_L}{R_L + 1k\Omega} \right) 50$$

or  $(R_L + 1k\Omega) V_z = 50 R_L$  or  $R_L V_z + 1k\Omega * V_z = 50 R_L$

But  $V_z = 10$  Then  $\Rightarrow 10 R_L + 10^3 \times 10 = 50 R_L$

$$40 R_L = 10000$$

$$R_{L \min} = \frac{10000}{40} = 250 \Omega$$

Then  $I_{L \max} = \frac{V_{RL \text{ or } V_z}}{R_{L \min}} = \frac{10}{250} = 40 \text{ mA}$

Step-II

But  $I_s = I_z + I_L = I_{z \max} + I_{L \min}$

So  $I_{L \min} = (I_s - I_{z \max}) = (I_s - 32 \text{ mA})$  — (1)

Find out  $I_s$  Write KVL in loop ①  $50 - 1k\Omega * I_s - 10 = 0$

$$I_s = \frac{50 - 10}{1k\Omega} = \frac{40}{10^3} = 40 \text{ mA}$$

Then  $I_{L \min} = 40 \text{ mA} - 32 \text{ mA} = 8 \text{ mA}$

For  $R_{L \max}$   $V_{RL} = I_L * R_L = V_z = 10$

$$R_L = \frac{10}{I_L} \text{ or } R_{L \max} = \frac{10}{I_{L \min}} = \frac{10}{8 \text{ mA}} = 1.25 k\Omega$$

$$R_{L \max} = 1.25 k\Omega$$

So Range of  $R_L \Rightarrow 250 \Omega$  to  $1.25 k\Omega$   
 Range of  $I_L \Rightarrow 8 \text{ mA}$  to  $40 \text{ mA}$  } Ans.

Part ② max wattage rating =  $I_{z \max} * V_z = 32 \text{ mA} \times 10 = 320 \text{ mWatt}$

2




Q In ckt zener breakdown voltage 6V and  $I_{ZK}$  current 5mA. Calculate the min load resistance & min power rating of the diode such that the o/p voltage remains constant at 6V.

Given:  $V_Z = 6V$ ,  $I_{ZK} = 5mA$

$$I_S = \frac{E_S - V_Z}{R_S} = \frac{10 - 6}{50} = 80mA$$

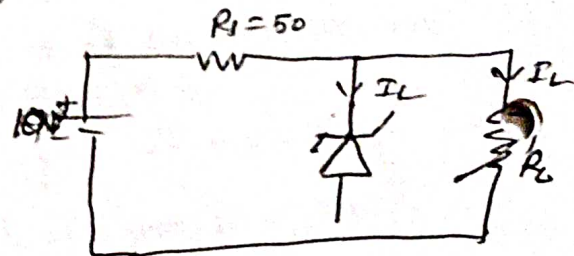When  $R_L$  is minimum then  $I_L$  is maximum.



$$I_{L(max)} = I_S - I_{Z(min)} = 80mA - 5mA = 75mA$$

$$\text{Then } R_L = \frac{V_L}{I_L} = \frac{V_Z}{I_L} \Rightarrow R_{L(min)} = \frac{V_Z}{I_{L(max)}}$$

$$R_{L(min)} = \frac{6}{75} = 80\Omega$$

$$P_{Z(min)} = V_Z \times I_{Z(min)} = 6 \times 5 = 30 \text{ watt}$$

If  $R_L$  is disconnected, load current become zero and zener current become maximum then

$$I_S = I_{Z(max)} + I_{L(min)} \Rightarrow I_{Z(max)} = I_S - I_{L(min)} = 80 - 0 = 80mA$$

$$P_{Z(max)} = V_Z \times I_{Z(max)} = 480mW$$

For a ckt zener diode has breakdown voltage 6V and  $I_{Z(\max)} = 5\text{mA}$  and a  $\max^m$  allowed power dissipation of 300mW. Calculate the Range of Load Current such that the o/p Voltage remains regulated at 6V.

Find out  $I_L \rightarrow$  Range

so when zener is ON

$$I_S = \frac{E_S - V_Z}{R_S} = \frac{9 - 6}{50} = 60\text{mA}$$


$$\text{But } I_S = I_Z + I_L = I_{Z\min} + I_{L\max} = I_{Z\max} + I_{L\min}$$

$$60\text{mA} = 5\text{mA} + I_{L\max}$$

$$I_{L\max} = 55\text{mA}$$

The Range of  $I_L$

$$10\text{mA to } 55\text{mA}$$

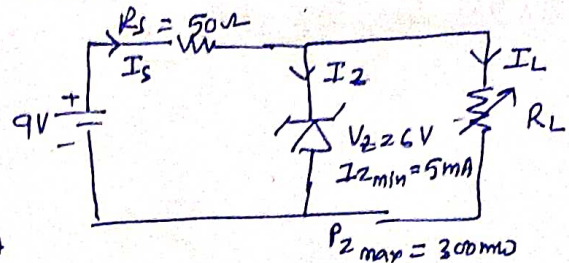

$$I_{Z\min} = I_S - I_{Z\max}$$

$$\text{But } P_{Z\max} = 300\text{mW} = I_{Z\max} \cdot V_Z$$

$$I_{Z\max} = \frac{300\text{mW}}{V_Z} = \frac{300\text{mW}}{6}$$

$$I_{Z\max} = 50\text{mA}$$

$$I_{L\min} = 60\text{mA} - 50\text{mA}$$

$$I_{L\min} = 10\text{mA}$$

③ Fixed  $R_L$ , variable ' $E_s$ ' The voltage ' $E_s$ ' must be large to turn on the zener diode. The minimum turn on voltage ( $E_{s(min)}$ ) is determined by -

$$V_L = V_Z = \left( \frac{R_L}{R_S + R_L} \right) * E_S \Rightarrow V_Z R_S + V_Z R_L = R_L E_S$$

$$E_{s(min)} = \frac{V_Z (R_S + R_L)}{R_L} \quad \text{--- (1)}$$

The max. value of  $E_S$  is limited by max. zener current  $I_{Zm}$ .

$$I_{Zm} = I_R - I_L \quad \text{or} \quad I_{R(max)} = I_{Zm} + I_L$$


$$E_{s(max)} = V_{R(max)} + V_Z$$

$$E_{s(max)} = I_{R(max)} * R_S + V_Z$$



When  $E_S \rightarrow$  Variable and  $R_L \rightarrow$  Fixed

Find out max & min value of  $I_Z$

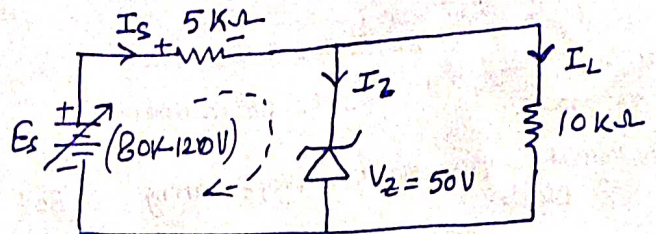

#  $I_S = I_Z + I_L$

But  $R_L$  is fixed, then value of  $I_L$  is also fixed.

to  $I_S \propto I_Z$  i.e. if  $I_S \uparrow$  then  $I_Z \uparrow$   
if  $I_S \downarrow$  then  $I_Z \downarrow$

When Zener is ON then  $V_{R_L} = V_Z = 10 k\Omega \times I_L$

But  $V_Z = 50V$ ; to  $I_L = \frac{50}{10 k\Omega} = 5 \text{ mA}$

Calculate the value of  $I_{Z \min}$  &  $I_{Z \max}$

$I_S = I_Z + I_L$

For  $I_{Z \min}$   $I_{S(\min)} = I_{Z \min} + I_L \Rightarrow I_{Z \min} = I_{S \min} - I_L$  — (1)

Find out  $I_{S \min}$  Write down KVL in first loop.

$E_S - I_S \times 5 k\Omega - 50 = 0$

$I_S = \frac{E_S - 50}{5 k\Omega}$  — (2)

From eqn (2) it is clear that  $I_S \propto E_S$  i.e. if  $E_{S \min}$  then  $I_{S \min}$

For  $I_{S \min}$  the value of  $E_S = 80V$  (Bcz  $E_S$  vary from  $80V$  to  $120V$ ) and  $E_{S \max}$  then  $I_{S \max}$

Then  $I_{S \min} = \frac{80 - 50}{5 k\Omega} = \frac{30}{5 k\Omega} = 6 \text{ mA}$

and  $I_{S \max} = \frac{120 - 50}{5 k\Omega} = \frac{70}{5 k\Omega} = 14 \text{ mA}$

from eqn (1)  $I_{Z \min} = I_{S \min} - I_L = 6 \text{ mA} - 5 \text{ mA} = 1 \text{ mA}$

$I_{Z \max} = I_{S \max} - I_L = 14 \text{ mA} - 5 \text{ mA} = 9 \text{ mA}$

Then range of  $I_Z = 1 \text{ mA}$  to  $9 \text{ mA}$

याद रख लो

(1)  $I_S = \frac{E_S - V_Z}{R_S}$

(2)  $I_S = I_Z + I_L$

(3)  $V_Z = V_{R_L} = \left( \frac{R_L}{R_L + R_S} \right) E_S$

(4)  $P_{Z \max} = I_{Z \max} \times V_Z$

(7) When Zener is off

$V_0 = V_{R_L} = \left( \frac{R_L}{R_L + R_S} \right) E_S$

(5) For Zener Conduction

$I_S \geq I_{Z \min} + I_L$

(6)  $E_{S \min} \geq \underbrace{(I_{Z \min} + I_L) R_S + V_Z}_{I_S R_S}$